

EE115B *Digital Circuits*

Instructor: Chenxi Xiao

Part of slides are from

© Pearson Education

Hengzhao Yang

Zhifeng Zhu

Yajun Ha




上海科技大学
ShanghaiTech University

ADC/DAC

Review of Op-Amps

Voltage follower

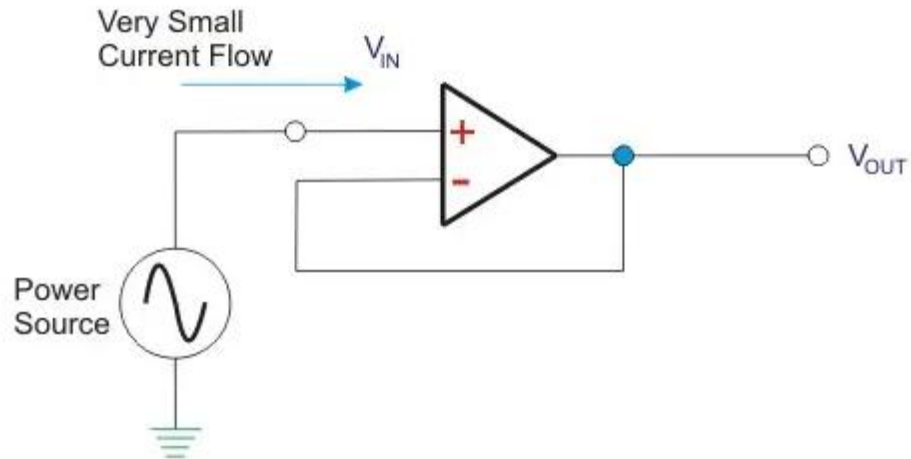- $V_{out}=V_{in}$
- Makes it possible to design circuits before/after amplifiers separately.
- Commonly used as output buffer (reduce output impedance)




Review of Op-Amps

Non-inverting amplifier

In non-inverting operational amplifier configuration, the input voltage signal, (V_{in}) is applied directly to the non-inverting (+) input terminal.
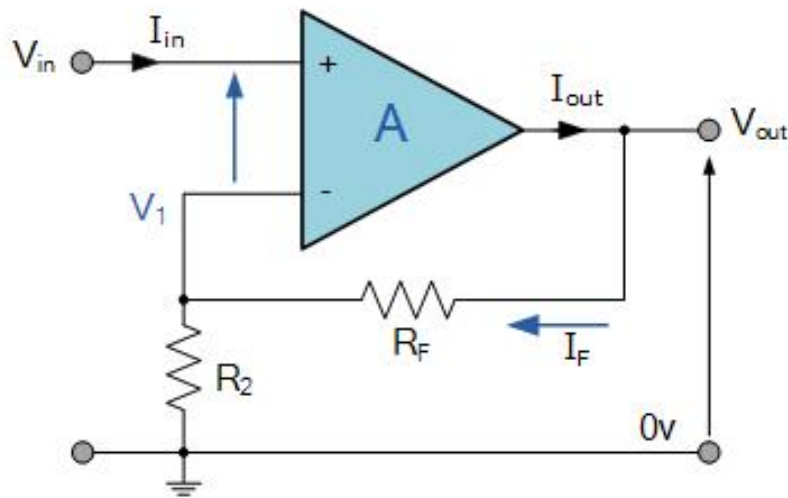
$$V_1 = \frac{R_2}{R_2 + R_F} \times V_{OUT}$$



Ideal Summing Point: $V_1 = V_{IN}$


Voltage Gain, $A_{(V)}$ is equal to: $\frac{V_{OUT}}{V_{IN}}$

$$\text{Then, } A_{(V)} = \frac{V_{OUT}}{V_{IN}} = \frac{R_2 + R_F}{R_2}$$

$$\text{Transpose to give: } A_{(V)} = \frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{R_2}$$

Review of Op-Amps


Inverting amplifier (with sum)

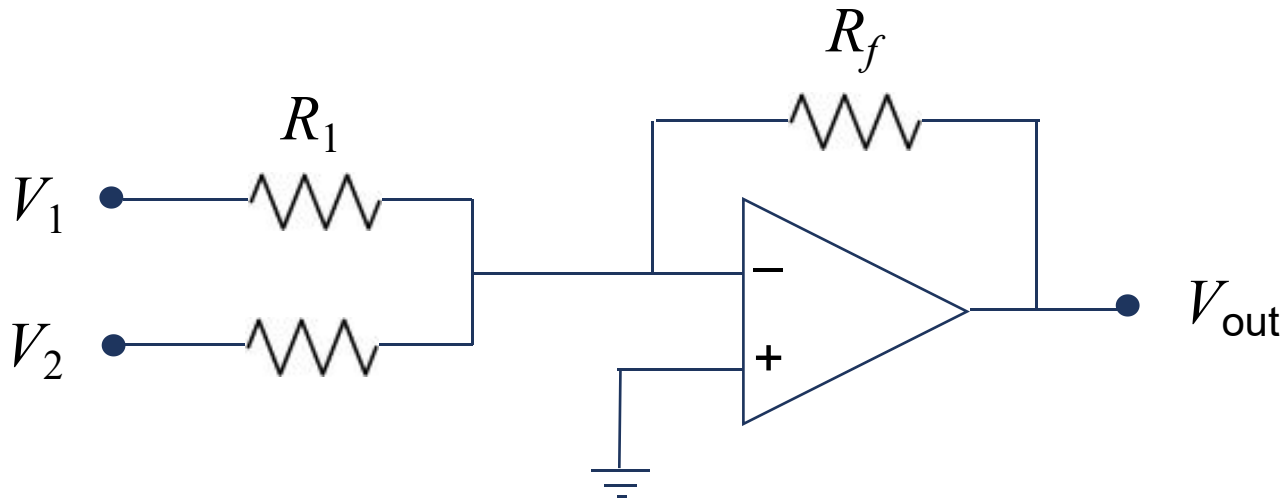

$$V_{out} = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2\right)$$



Review of Op-Amps

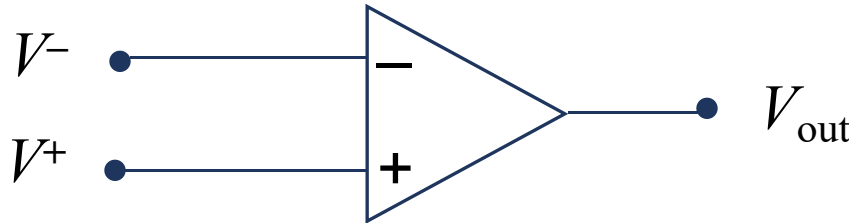


In the linear region

$$V_{out} = A(V^+ - V^-)$$

A is huge (10^5 or larger)
for DC component

In saturation
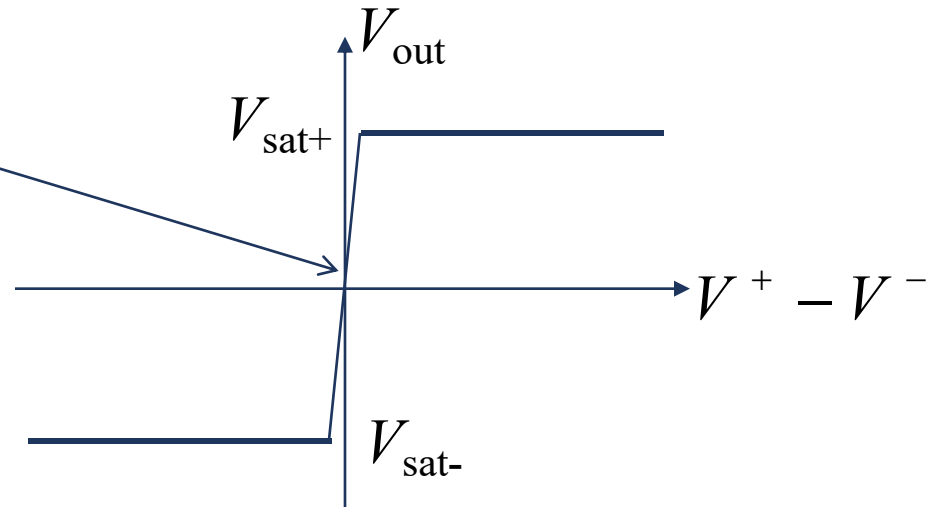
$$V_{out} = \begin{cases} V_{sat+} & \text{if } V^+ > V^- \\ V_{sat-} & \text{if } V^+ < V^- \end{cases}$$



(V_{sat+} and V_{sat-} are largely
determined by power supplies.)



→ essentially **digital output** because the linear region is tiny



Review of Op-Amps

Using an Op Amp as a Comparator

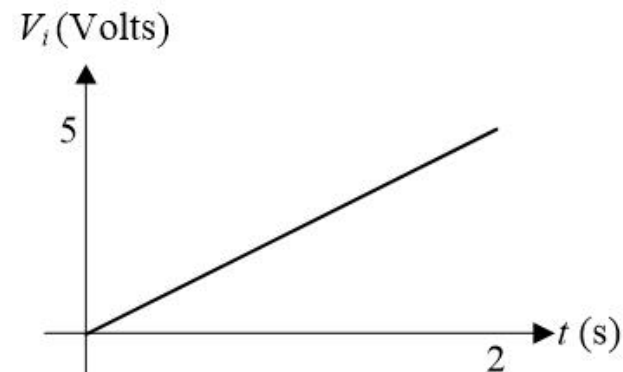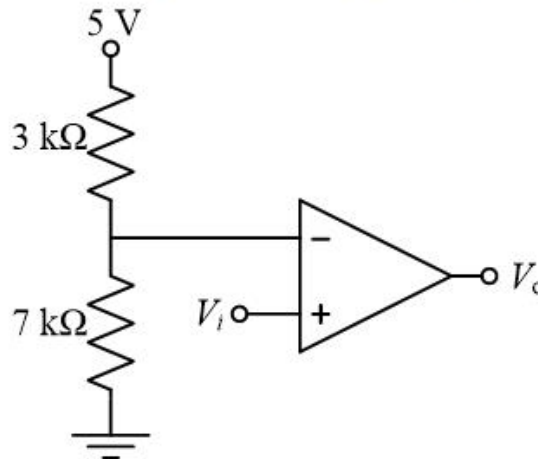In the circuit below, the analog voltage V_i varies linearly from 0 V to 5 V. Graph the output, V_o , from $t = 0$ to $t = 2$ s. Assume the positive and negative saturation voltages of the op amp are +15 V and -15 V, respectively.



Solution


$$V^- = \text{voltage at inverting terminal} = \left(\frac{7\text{ k}\Omega}{7\text{ k}\Omega + 3\text{ k}\Omega} \right) 5 = 3.5 \text{ V}$$

$$\Rightarrow V_o \approx \begin{cases} -15 \text{ V, if } V_i < 3.5 \text{ V} \\ +15 \text{ V, if } V_i > 3.5 \text{ V} \end{cases} \Rightarrow V_o \approx \begin{cases} -15 \text{ V, } 0 < t < 1.4 \text{ s} \\ +15 \text{ V, } 1.4 < t < 2 \text{ s} \end{cases}$$




DAC: Binary-Weighted-Input DAC

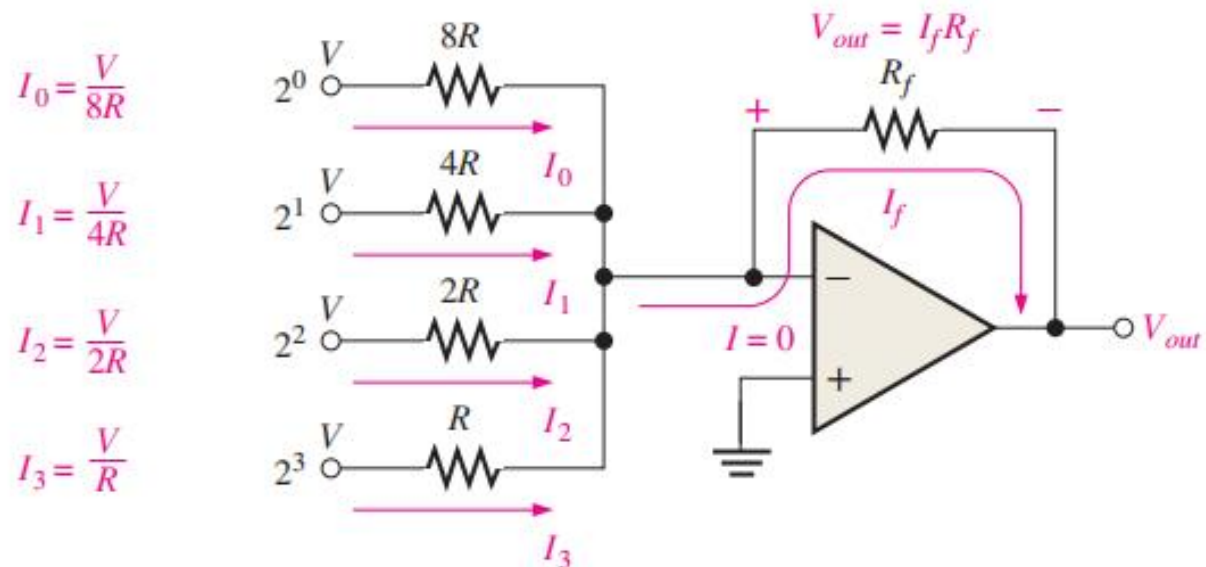Uses a resistor network with resistance values that represent the binary weights of the input bits of the digital code.



DAC: Binary-Weighted-Input DAC

Example: 4-bit ADC

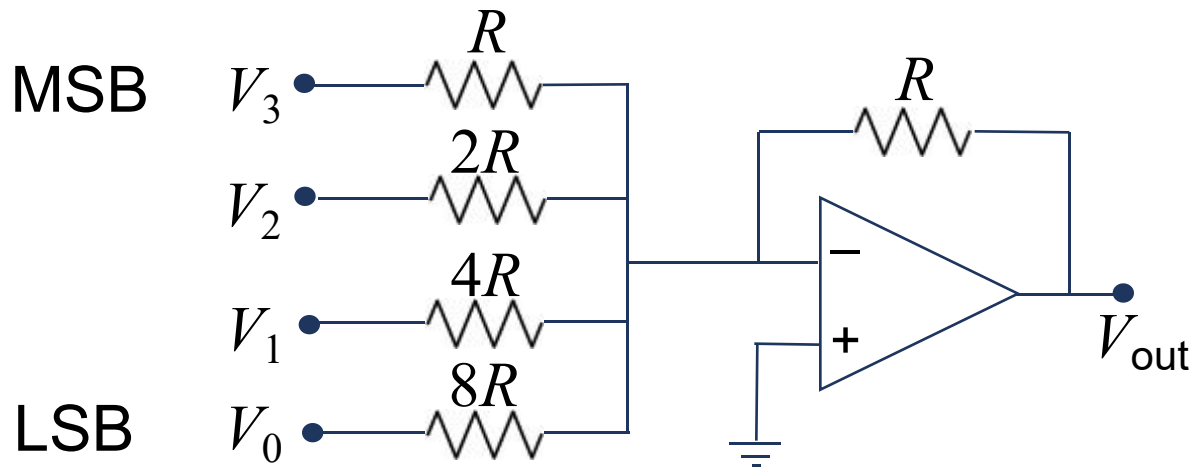

Binary input: $b_3b_2b_1b_0$

Assume

$$V_i = \begin{cases} V_H, & \text{if } b_i = 1 \\ 0, & \text{if } b_i = 0 \end{cases}$$

Equivalently, $V_i = b_i V_H$

Goal: Verify that this is a DAC (verify that V_{out} is proportional to input word value).

$$V_{out} = - \left(V_3 + \frac{V_2}{2} + \frac{V_1}{4} + \frac{V_0}{8} \right) =$$

$$= -V_H/8(2^3b_3 + 2^2b_2 + 2^1b_1 + 2^0b_0) \quad V_H \text{ is high logic voltage}$$

$$= \text{constant} * (\text{decimal value of binary input})$$

ADC


ADC 1: Flash ADC

In general, $2^n - 1$ comparators are required for conversion to an n-bit binary code

- Needs lots of comparators.
- Ultra-fast
- How to design a priority encoder?


Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

V: valid or not

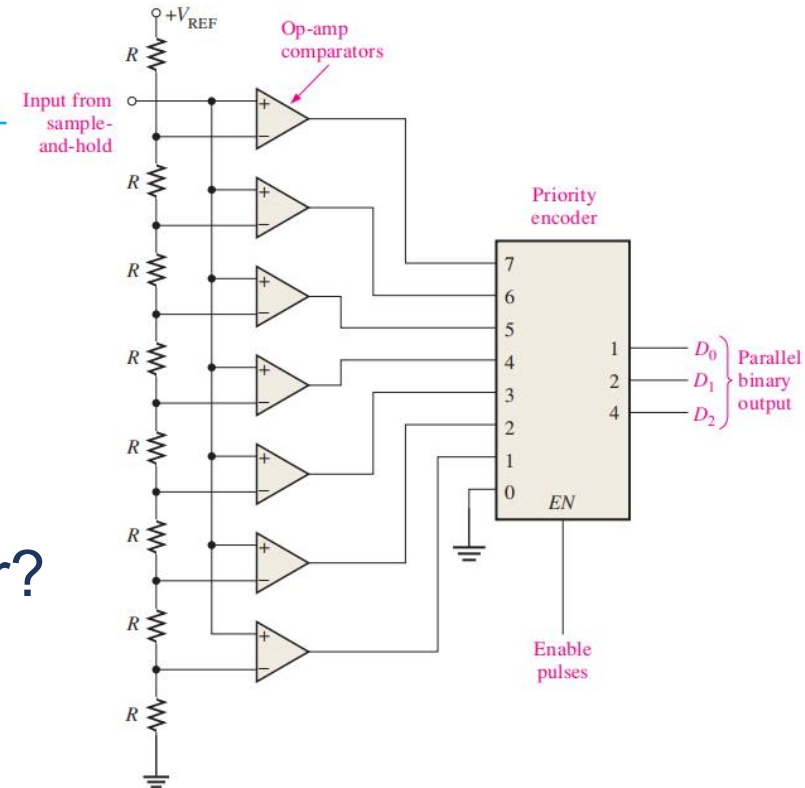

ADC 1: Successive-Approximation ADC

The input bits of the DAC are enabled (made equal to a 1) one at a time. So that V_{out} is getting close to V_{in} .

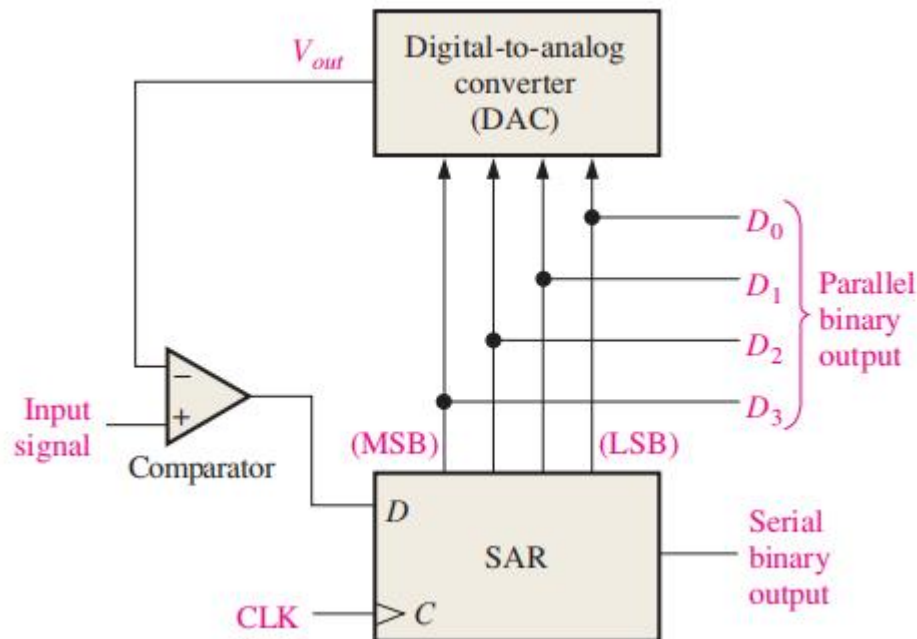

ADC 2: Successive-Approximation ADC

Assume $V_{ref}=15V$

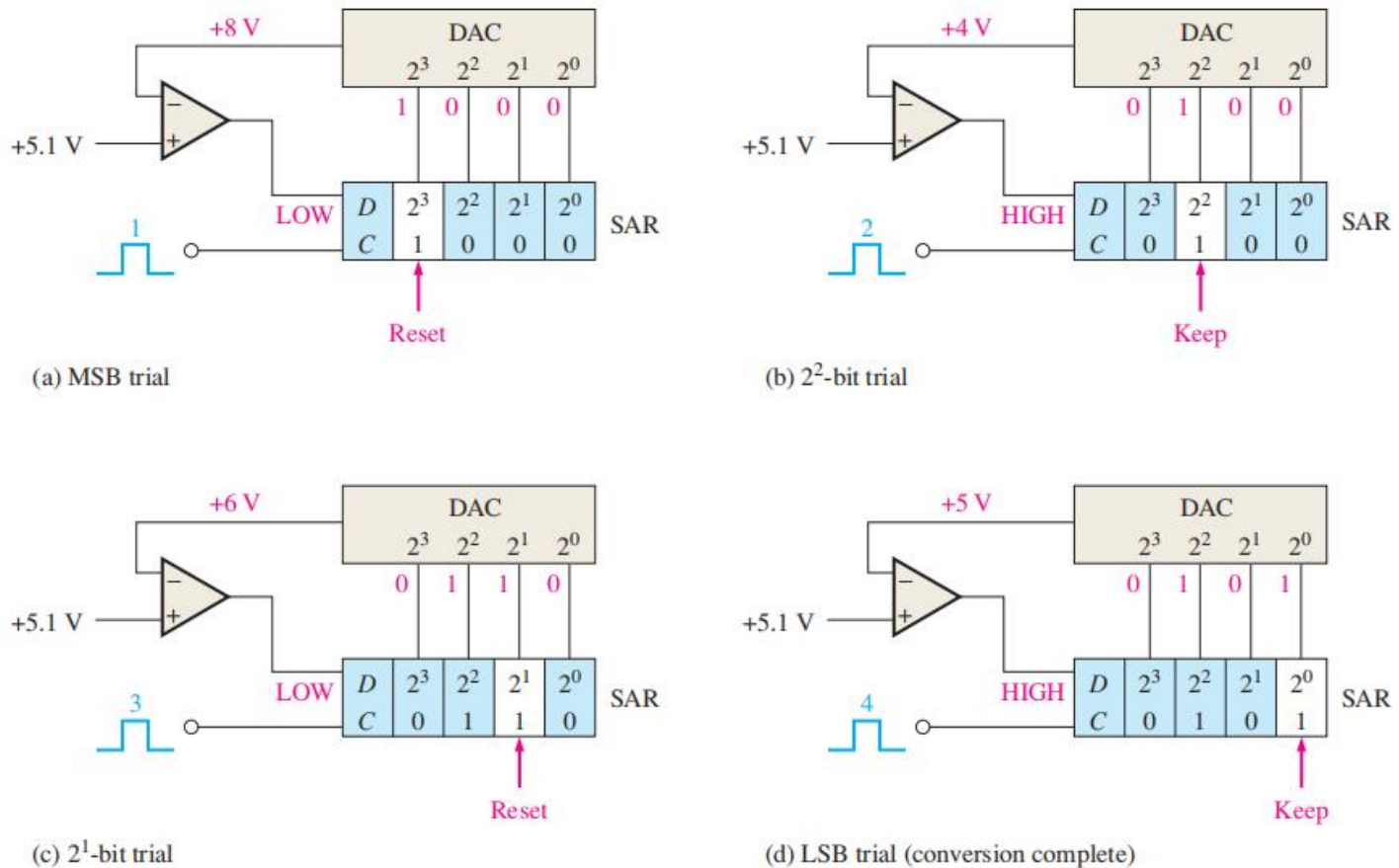




FIGURE 12-18 Illustration of the successive-approximation conversion process.

Quantization

- Quantization** is the process of mapping a continuous range of analog input values to a finite set of digital levels.
- Resolution**: with N bits, the ADC/ADC can represent 2^N distinct levels.

$$\text{LSB (or resolution)} = \frac{V_{ref}}{2^N}$$

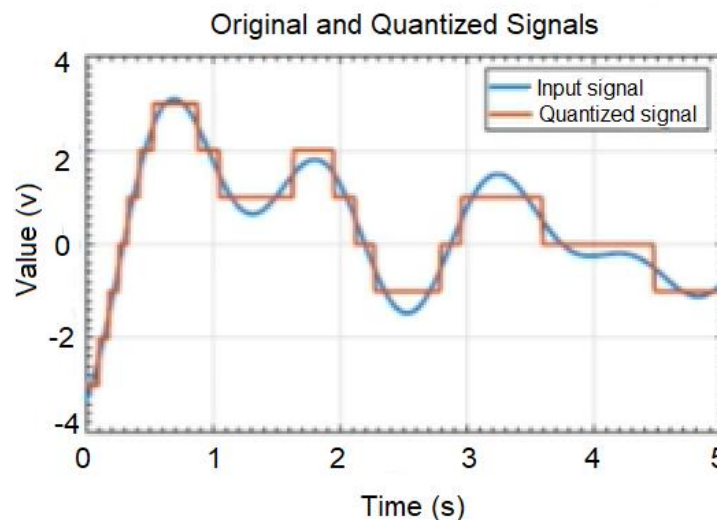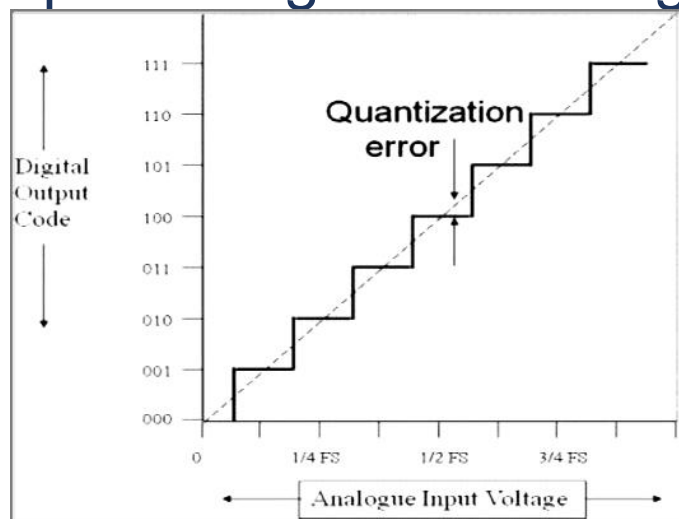- Quantization error**: difference between the actual analog input voltage and the digitized output voltage produced.



Quantization

Suppose you have a 3-bit ADC with:

- $V_{ref} = 8\text{ V}$
- Number of levels = $2^3 = 8$
- $\text{LSB} = \frac{8\text{ V}}{8} = 1\text{ V}$

Then:

- Input voltage of 2.6 V gets quantized to 3 V (nearest digital level).
- Quantization error = $3\text{ V} - 2.6\text{ V} = \mathbf{+0.4\text{ V}}$
- The maximum possible error = $\pm 0.5\text{ V}$ (which is $\pm \frac{1}{2}$ LSB)



Fourier Transform

Fourier transform is a tool that allows us to represent a real-valued function as a superposition (sum/integral) of sines and cosines with suitably-chosen amplitudes and frequencies

Fourier series

$$g(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos(n\omega t) + b_n \sin(n\omega t)]$$


Fourier Coefficients

$$a_n = \frac{2}{T} \int_0^T g(t) \cos(n\omega t) dt$$

$$b_n = \frac{2}{T} \int_0^T g(t) \sin(n\omega t) dt$$

Fourier Transform
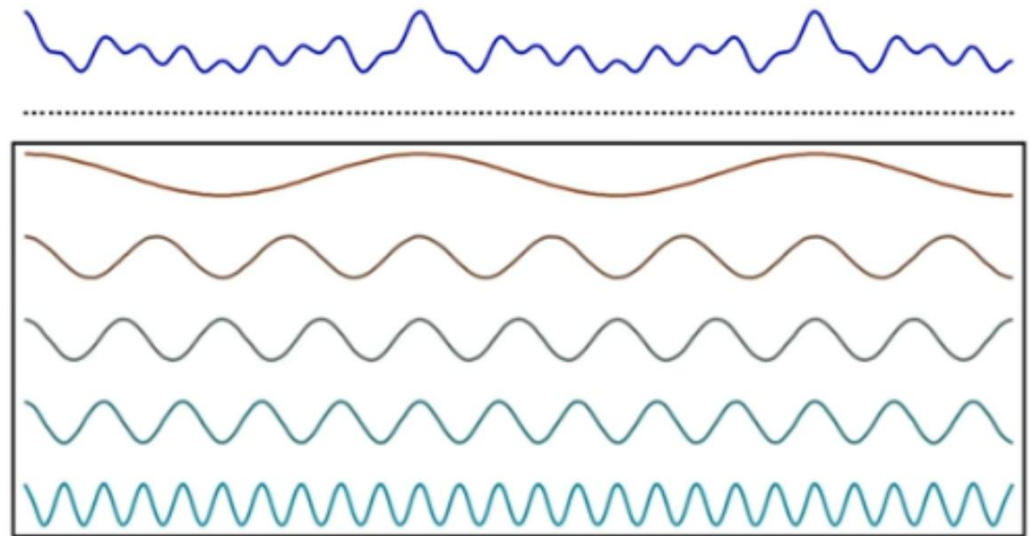
$$G(f) = \int_{-\infty}^{\infty} g(t) (\cos(2\pi f t) + i \sin(2\pi f t)) dt$$



FT: continuous, aperiodic

(If you want to know its principle, take EE150: Signals and Systems)




Nyquist-Shannon Sampling Theorem

An analog signal must be sampled at least twice as fast as the bandwidth of the signal to accurately reconstruct the waveform; otherwise, the high-frequency content creates an alias at a frequency inside the spectrum of interest (passband).

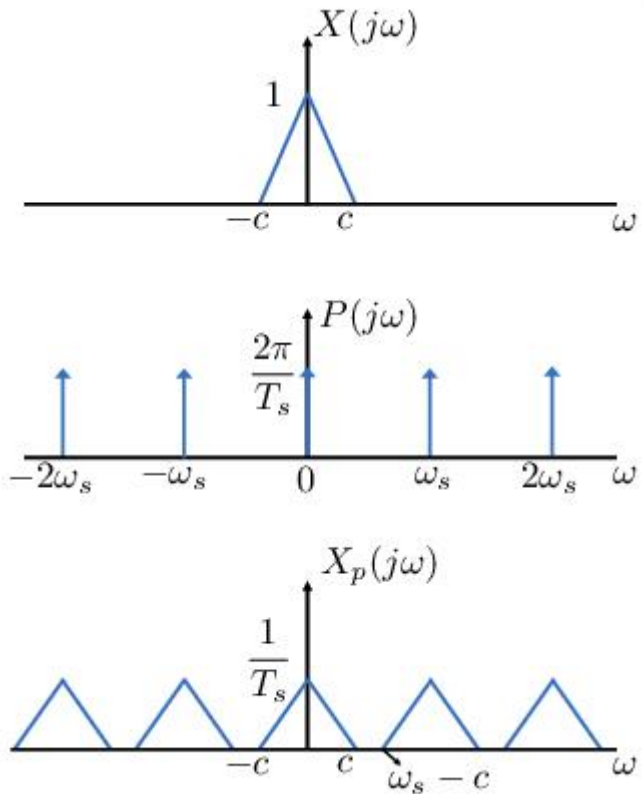Example:

- Suppose you're sampling audio with frequency content up to 20 kHz.
- To preserve the signal, you must sample at at least 40 kHz (usually 44.1 kHz or 48 kHz in practice).
- An anti-aliasing low-pass filter with a cutoff around 20 kHz is added.



What's next?

Courses:

- Provided by SIST: 数字集成电路、CA、FPGA、嵌入式系统、板级电路设计实践、...
- 一生一芯: <https://ysyx.oscc.cc/>

Activities:





- Electronic Competition
- RoboMaster
- InterStudio
- Research Intern in SIST Labs
- ...




Our lab has openings for undergraduate internship students

Research Interests: Tactile Perception, Robot Interaction, Robot Manipulation

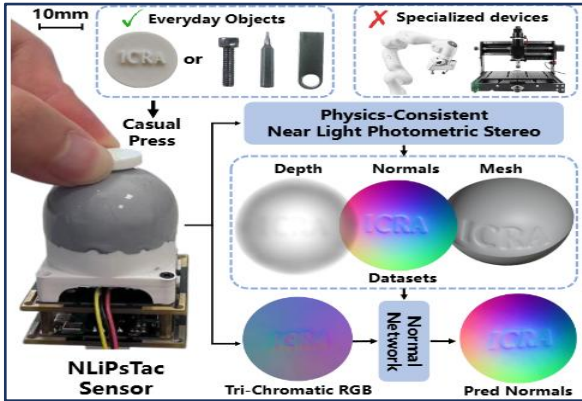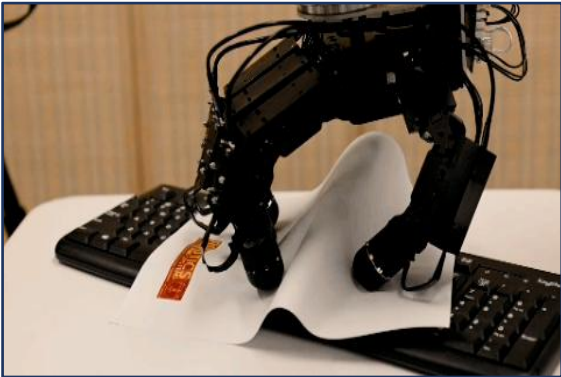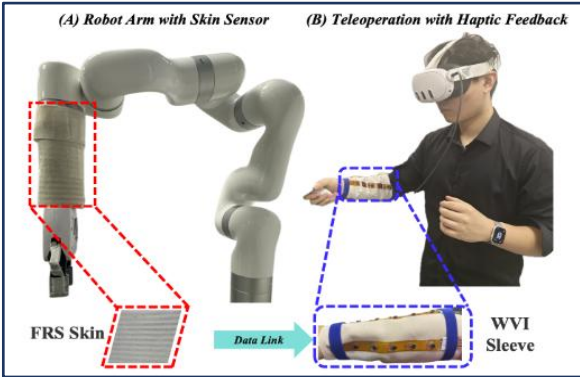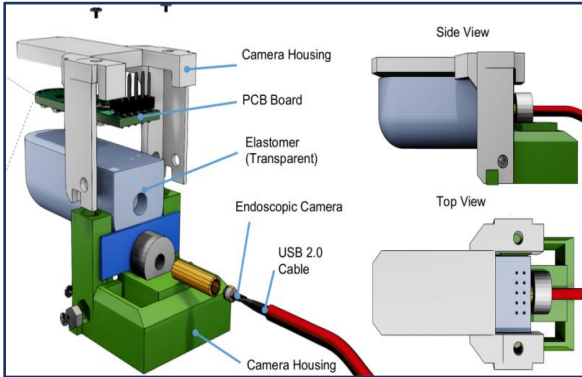
Location: SIST 1D-301A 1D-303, inquiry via email: xiaochx@shanghaitech.edu.cn



Tactile Perception

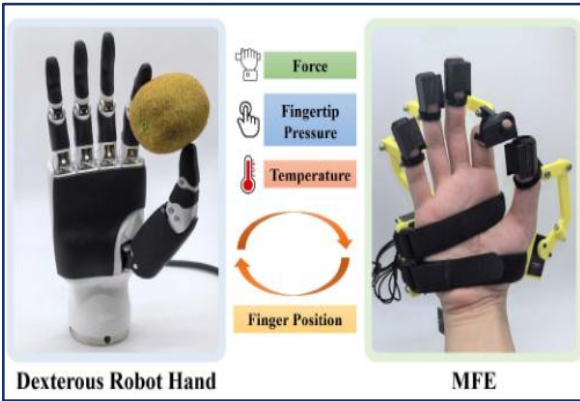

Robot Interaction

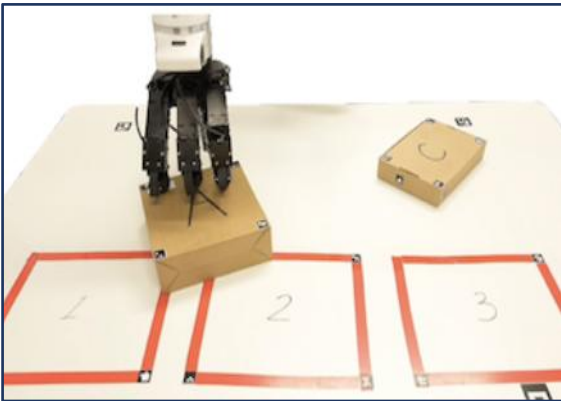

Manipulation